

Capacitance Tutorial

-

Parallel Capacitance Circuits

When two capacitor are connected in Parallel, The equivalent capacitance is given by

$$C=C_1 + C_2$$

The voltage is same across the both the capacitor but charge is not and it depends on the capacitance

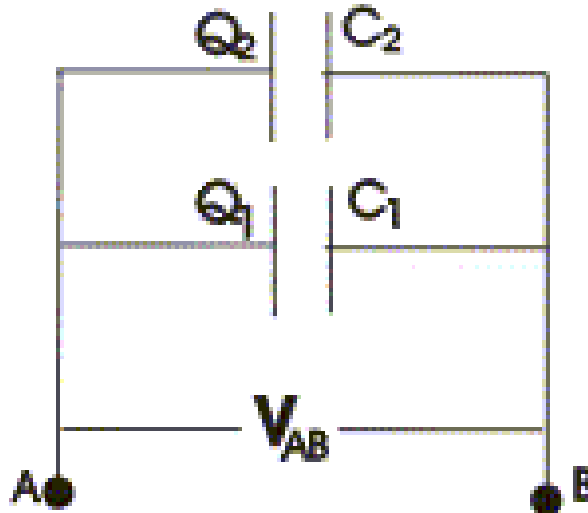


Figure 6

Series Capacitance Circuits

When two capacitor are connected in series , the equivalent capacitance is given by

$$1/C=1/C_1+1/C_2$$

The charge on the both the capacitor is same but Voltage is different

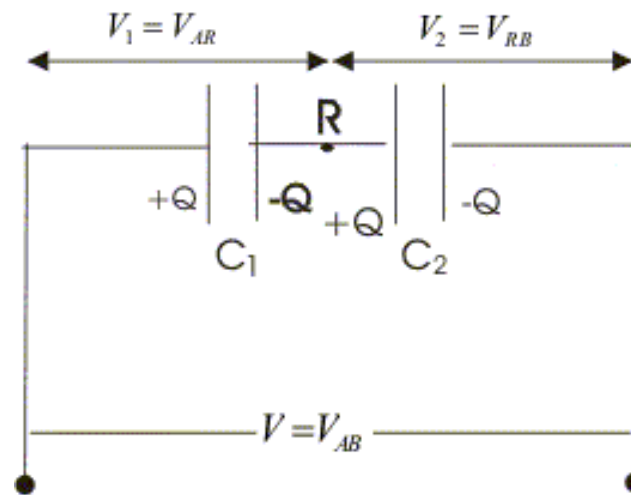



Figure 7

Capacitance Question

Find the equivalent capacitance of the circuit?

Find the charge on the capacitor C_1 ?

Given $C_1 = C_2 = C_3 = C$

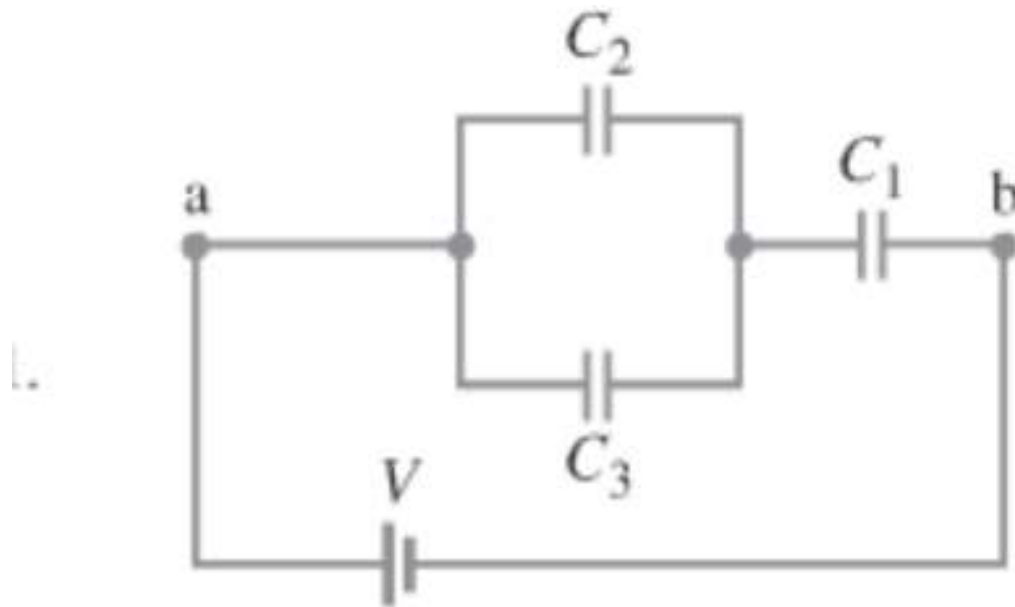


Solution

We need to make of parallel series capacitance formula as stated in previous slide

The Capacitor C_2 and C_3 are in parallel , So we can replace those capacitor by the equivalent capacitance

$$C_{23} = C_2 + C_3 = 2C$$

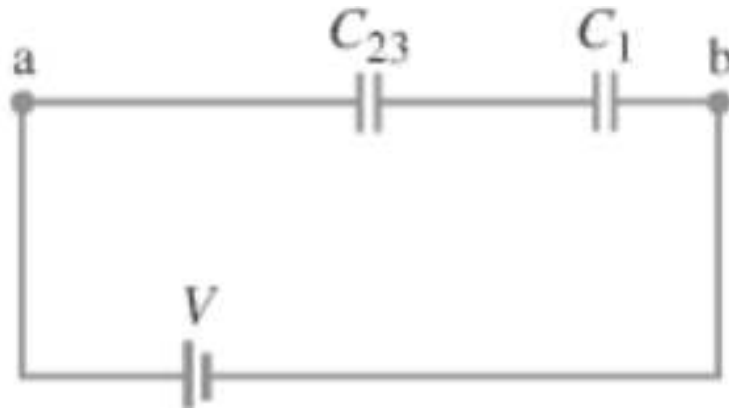


•

Solution Continued

Now C_{23} and C_1 are in series, So we can replace those capacitor by the equivalent capacitance
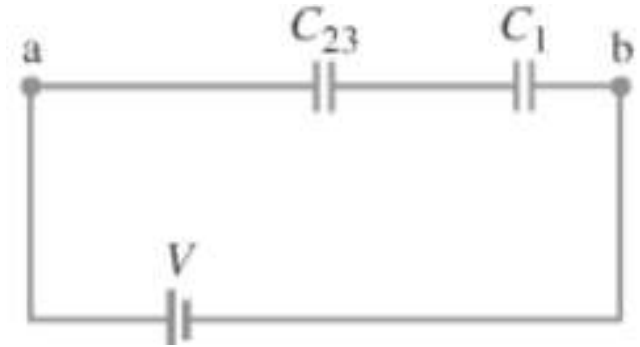
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{23}} = \frac{1}{C} + \frac{1}{2C} = \frac{3}{2C}$$



$$C_{eq} = 2C/3$$

Now total charge in the circuit (Q) = $C_{eq}V = 2CV/3$.

Now since C_1 is in series with the whole circuit, The charge on C_1 will be $2CV/3$

•

*For more tips and study
material please visit our
website
<http://physicscatalyst.com>*