

## Numerical Questions for Electricity

1) A wire of length 3 m and area of cross-section  $1.7 \times 10^{-6} \text{ m}^2$  has a resistance  $3 \times 10^{-2} \text{ ohm}$ .

a) What is the formula for resistivity of the wire and what is the unit of it

b) Calculate the resistivity of the wire

**Ans)**

a) Resistivity of the wire is given by

$$\rho = \frac{RA}{L}$$

And It unit is Ohm-m

b) In this case

$L=3 \text{ m}$

$A=1.7 \times 10^{-6} \text{ m}^2$

$R=3 \times 10^{-2} \text{ ohm}$

So

$\rho=1.7 \times 10^{-8} \text{ Ohm-m}$

2) The table given below shows the resistivity of three Material X, Y and Z?

Samples	X	Y	Z
Resistivity	$3 \times 10^{-9}$	$11.1 \times 10^{-6}$	$18 \times 10^{-17}$

a) Arrange the samples in increasing order of conductivity

b) Which of these is best conductor?

c) Which are these is best insulator?

This material is created by <http://physicscatalyst.com/> and is for your personal and non-commercial use only.

**Ans)**

a) Conductivity is inversely proportional to resistivity

So

$$Y < X < Z$$

b) Z is the best conductor as it has least resistivity

c) Y is the best insulator as it has highest resistivity

**3)** There are m resistor each of resistance R. First they all are connected in series and equivalent resistance is X. Now they are connected in parallel and equivalent resistance is Y. What is the ratio of X and Y?

**Ans)**

Series combination

$$X = R + R + R + \dots = mR$$

Parallel combination

$$\frac{1}{Y} = \frac{1}{R} + \frac{1}{R} + \dots = \frac{m}{R}$$

Or  $Y = R/m$

So  $X : Y = m^2 : 1$

**4)** We have four resistors A ,B ,C and D of resistance 4ohm,8ohm ,12 ohm and 24 ohm respectively?

1	Lowest resistance which can be obtained by combining these four resistors	
2	highest resistance which can be obtained by	

	combining these four resistors	
--	--------------------------------	--

**Ans)**

Lowest resistance is obtained in parallel combination

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{8} + \frac{1}{12} + \frac{1}{24}$$

Or  $R=2\Omega$

Highest resistance is obtained in series combination

$$R=4+8+12+24=64\Omega$$

5) Three resistors  $5\Omega$ ,  $10\Omega$  and  $30\Omega$  are connected in parallel with the battery of Voltage  $6V$ ?

S.no	Questions	
1	The value of current across each resistor	
2	The value of Potential difference across each resistor	
3	Total current in the circuit	
4	Effective resistance of the circuit	

**Ans)**

Potential difference remains same across parallel combination

So current in each resistor is calculated as

$$I_1 = V/R_1 = 6/5 = 1.2 \text{ A}$$

$$I_2 = V/R_2 = 6/10 = .6 \text{ A}$$

$$I_3 = V/R_3 = 6/30 = .2 \text{ A}$$

Total current in the circuit

$$I = I_1 + I_2 + I_3 = 1.2 + .6 + .2 = 2 \text{ A}$$

Effective resistance

$$\frac{1}{R} = \frac{1}{5} + \frac{1}{10} + \frac{1}{30}$$

$$\Rightarrow R = 3\Omega$$

6) An electric bulb draws a current of .8 A and works on 250 V on the average 8 hours a day.

a) Find the power consumed by the bulb

b) If the electric distribution company charges Rs 5 for 6 KWH, what is the monthly bill for 60 days

**Ans)** Power of the electrical bulb is given by


$$P = V \times I = .8 \text{ A} \times 250 \text{ V} = 200 \text{ W} = .2 \text{ KW}$$

Total energy consumption by the bulb in 60 days

$$E = P \times t = .2 \times 8 \times 60 = 96 \text{ KWH}$$

$$\text{So cost will be} = 5 \times 96 / 6 = 80 \text{ Rs}$$

7)

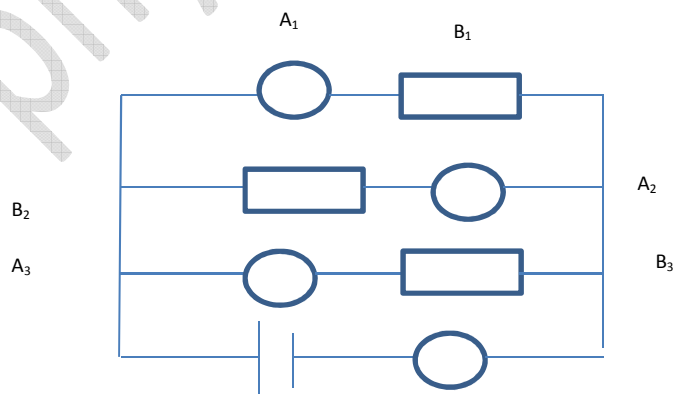

A

$A_1, A_2, A_3$  and A are ammeters connected in the circuit

$B_1, B_2$  and  $B_3$  are three identical bulbs

They all are connected to Voltage source as shown in Figure

When the three bulb are working good and glowing ,the current recorded in Ammeter A is 6 A

**Answer Following questions**

- Same amount of current will go through each Bulb. And the value is 2 A .True or False
- If the Bulb  $B_3$  is blown away, the bulb  $B_1$  and  $B_2$  will start glowing more. True or False
- What will happen to all the ammeter reading if Bulb  $B_1$  is blown away
- The current shown in Ammeter A remains even any bulb goes down. True or False

**Ans)**

a) Since Bulb are identical and connected in parallel with Voltage. Same current will flow through each bulb. Since the total current is 6 A. Individual current will be 2 A

b) If the Bulb  $B_3$  is blown away, The potential difference across other bulb still remains same, So same current will flow and they will glow as it is. No change

c) when Bulb  $B_1$  goes down, the current in that part become zero.

So reading of Ammeter  $A_1$  becomes zero

Reading of Ammeter  $A_2$  will remain same i.e. 2 A

Reading of Ammeter  $A_3$  will remain same i.e. 2 A

Reading of Ammeter A will be =  $2+2=4$  A

d) As shown above, the reading of Ammeter A will change

**8) Gave the formula for each**

1	Ohm's Law	
2	Resistance in terms of Length,Area,resistivity	
3	Current in terms of Resistance and Voltage	
4	Equivalent Resistance for Resistors in Series	
5	Equivalent Resistance for Resistors in Parallel	
6	Power produced in the resistance	

### Solutions

1	Ohm's Law	$V=IR$
2	Resistance in terms of Length,Area,resistivity	$R = \rho \frac{L}{A}$
3	Current in terms of Resistance and Voltage	$I = \frac{V}{R}$
4	Equivalent Resistance for Resistors in Series	$R=R_1+R_2+R_3,\dots$
5	Equivalent Resistance for Resistors in Parallel	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$
6	Power produced in the resistance	$P=I^2R$